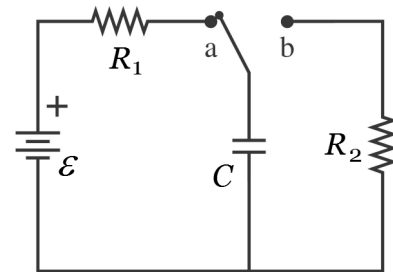



Example

The capacitor in the illustrated circuit is initially uncharged. The switch is placed in position a for $20\ \mu\text{s}$, then thrown to position b . What is the current through the resistor R_2 $10\ \mu\text{s}$ after the switch is in position b ? $\mathcal{E} = 9.0\ \text{V}$, $C = 1.0\ \mu\text{F}$, $R_1 = 20\ \Omega$, and $R_2 = 10\ \Omega$.



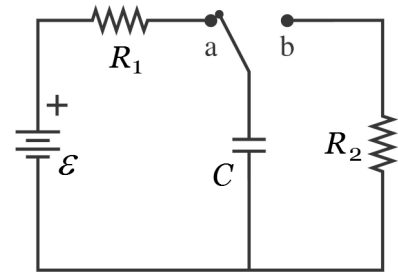
Problem

The capacitor in the illustrated circuit is initially uncharged. The switch is placed in position a for 2.0 ms , then thrown to position b . How much energy is dissipated in the resistor R_2 during the first 4.0 ms that the switch is in position b ? $\mathcal{E} = 50\text{ V}$, $C = 20\text{ }\mu\text{F}$, $R_1 = 200\text{ }\Omega$, and $R_2 = 100\text{ }\Omega$.



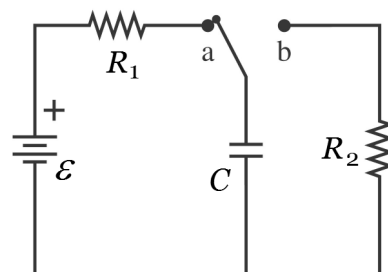Example

The capacitor in the illustrated circuit is initially uncharged. The switch is placed in position a for $20\ \mu\text{s}$, then thrown to position b . What is the current through the resistor R_2 $10\ \mu\text{s}$ after the switch is in position b ? $\mathcal{E} = 9.0\ \text{V}$, $C = 1.0\ \mu\text{F}$, $R_1 = 20\ \Omega$, and $R_2 = 10\ \Omega$.



While the switch is in position a :

$$\begin{aligned}\tau_1 &= R_1 C = 20\ \Omega \cdot 1\ \mu\text{F} = 20\ \mu\text{s} \\ Q &= Q_0 (1 - e^{-\frac{t}{\tau_1}}) \\ &= C V (1 - e^{-\frac{20\ \mu\text{s}}{20\ \mu\text{s}}}) = 1\ \mu\text{F} \cdot 9\text{V} (1 - e^{-1}) \\ &= 9\ \mu\text{C} (1 - e^{-1}) \\ &= 9(1 - e^{-1})\ \mu\text{C}.\end{aligned}$$


While the switch is in position b :

$$\begin{aligned}Q' &= Q e^{-\frac{t}{\tau_2}} \\ &= (9(1 - e^{-1})\ \mu\text{C}) \cdot e^{-\frac{10\ \mu\text{s}}{10\ \mu\text{s}}} \\ &= 9(1 - e^{-1}) e^{-1}\ \mu\text{C} = 2.09\ \mu\text{C} \\ I &= \frac{dQ'}{dt} = \left(-\frac{1}{\tau_2}\right) Q e^{-\frac{t}{\tau_2}} \Big|_{t=10\ \mu\text{s}} = \left(-\frac{1}{10\ \mu\text{s}}\right) (9(1 - e^{-1})\ \mu\text{C}) e^{-1} \\ &= 0.209\ \frac{\text{C}}{\text{s}} = 209\ \text{A}\end{aligned}$$

($\tau_2 = R_2 C = 10\ \Omega \cdot 1\ \mu\text{F} = 10\ \mu\text{s}$)

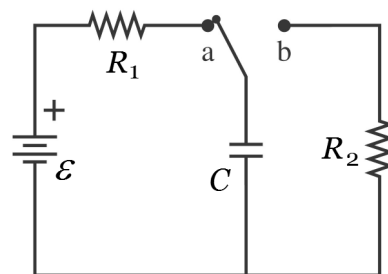Problem

The capacitor in the illustrated circuit is initially uncharged. The switch is placed in position a for 2.0 ms , then thrown to position b . How much energy is dissipated in the resistor R_2 during the first 4.0 ms that the switch is in position b ? $\mathcal{E} = 50\text{ V}$, $C = 20\text{ }\mu\text{F}$, $R_1 = 200\text{ }\Omega$, and $R_2 = 100\text{ }\Omega$.



when switch is on a .

$$\tau_1 = R_1 C = 200\Omega \cdot 20\mu\text{F} = 4000\mu\text{s} = 4\text{ ms}$$

$$Q = Q_0 (1 - e^{-\frac{t}{\tau_1}}) = C \mathcal{E} (1 - e^{-\frac{t}{\tau_1}})$$

$$= 20\mu\text{F} \cdot 50\text{V} (1 - e^{-\frac{1}{2}})$$

$$= 1000\mu\text{C} (1 - e^{-\frac{1}{2}})$$

when switch on b .

$$Q' = Q e^{-\frac{t}{\tau_2}} = Q e^{-\frac{t}{R_2 C}} = Q e^{-\frac{4\text{ ms}}{100\Omega \cdot 20\mu\text{F}}}$$

$$= Q e^{-2}$$

$$\Delta E = \frac{1}{2} \frac{Q^2}{C} - \frac{1}{2} \frac{Q'^2}{C} = \frac{1}{2} \frac{Q^2}{C} (1 - (e^{-2})^2)$$

$$= \frac{1}{2} \frac{(1 - e^{-4})}{C} (1000\mu\text{C} (1 - e^{-\frac{1}{2}}))^2$$

$$= \frac{1}{2} \frac{(1 - e^{-4}) (1000\mu\text{C} (1 - e^{-\frac{1}{2}}))^2}{20\mu\text{F}}$$

$$\Delta E = \frac{1}{2} \frac{0.1519\text{ C}^2}{20\text{ F}} = 0.0038\text{ J}$$